TI Designs IO-Link PHY BoosterPack



TI Designs

TI Designs provide the foundation that you need including methodology, testing, and design files to quickly evaluate and customize the system. TI Designs help *you* accelerate your time to market.

Design Resources

TIDA-00339 Design Folder
SN65HVD102 Product Folder
TPS7A1633 Product Folder
MSP-EXP430FR4133 Tool Folder
TI LaunchPad Ecosystem Tool Folder




ASK Our E2E Experts
WEBENCH® Calculator Tools

Design Features

- IO-Link V1.1 and V1.0 Connectivity Out-of-the-Box (TMG Stack, Physical Interface Device (PHY), and M12 Connector)
- Simple Interfacing of Sensors
- Designed to Meet With: IEC 61000-4-2, IEC 61000-4-4, IEC 61000-4-5, and IEC 60255-5 Standards

Featured Applications

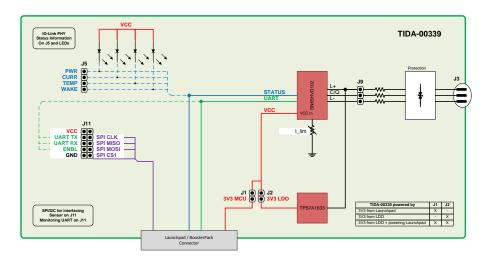- Sensors and Field Transmitters
- Factory Automation and Process Control
- Field Actuators
- Building Automation
- Portable Instrumentation





All trademarks are the property of their respective owners.





An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Key System Specifications

PARAMETER		SPECIFICATION
IO-Link Version		V1.1 (Compatible to V1.0)
IO-Link	SIO Mode	Supports SIO Mode
	BAUD Rate Support	COM1, COM2, and COM3
Designe	d to Standards	IEC 61000-4-2, IEC 61000-4-4, IEC 61000-4-5, and IEC 60255-5
Modu	ılar Design	Easy to use with existing LaunchPads
Sensor Front-End		SPI or I ² C Interface for sensor via BoosterPack or external
IO-	Link PHY	Easy access to all signals of IO-Link PHY (SN65HVD102)



www.ti.com System Description

2 System Description

The TI design TIDA-00339 is a fully IO-Link compliant design enabling the user to easily evaluate the IO-Link communication. The modular approach is capable of use with different MCUs (microcontrollers) based on the LaunchPad and BoosterPack ecosystem and also allows the user to test his or her own sensor front-end.

2.1 IO-Link Interface

The system incorporates an IO-Link PHY plus protection circuit (bypassable) and a standard M12, 4-pin, A-coded connector, which can be connected to any IO-Link master system and supports IO-Link V1.1 and V1.0.

The design also allows use of the IO-Link PHY in SIO Mode, either manually (through the switch button) or through MCU communication.

2.2 Power Supply

A high input voltage, low-dropout regulator (LDO) (V_{IN_max} = 60 V) can generate 3.3-V VCC of the system directly from the nominal 24 V of the IO-Link L+ line, while withstanding potential high voltage inputs during surge conditions. Alternatively, the connected LaunchPad can power the system.

2.3 TI LaunchPad and BoosterPack Ecosystem

TIDA-00339 must be used in combination with an MCU, on which the IO-Link stack is running. The advantage of the design in the BoosterPack pin-out is the flexible option of using an MCU that best suits the needs of the customer. Many TI MCUs are available as a LaunchPad, which can easily connect to the IO-Link PHY BoosterPack design.

This design guide uses the LaunchPad MSP-EXP430FR4133 to showcase features.

View further information on TI's LaunchPad and BoosterPack ecosystem here: www.ti.com/launchpad.

2.4 Sensor Front-End

In addition to the actual IO-Link PHY evaluation, the system allows users to attach their own sensor frontends with a serial peripheral interface (SPI) or I²C interface. Two options are available for the user:

- 1. Sensor attach through headers: the TI design provides easy access to the MCUs SPI and I²C interface on the board. An external sensor front-end with an SPI or I²C interface can be connected.
- Sensor attach through BoosterPack: the LaunchPad ecosystem allows the connection of several BoosterPacks. This design also allows an additional BoosterPack (containing a sensor front-end) to stack up and communicate with the MSP430™ of the LaunchPad. For example, the TIDA-00168 Thermocouple AFE has been developed to also be used as a BoosterPack.



Block Diagram www.ti.com

3 Block Diagram

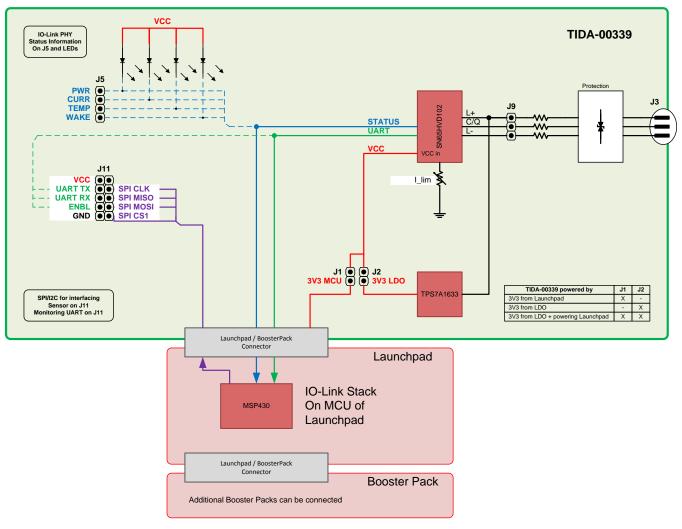


Figure 1. TIDA-00339 System Block Diagram

3.1 Highlighted Products

3.1.1 SN65HVD102

The SN65HVD101 and SN65HVD102 IO-Link PHYs implement the IO-Link interface for industrial point-to-point communication. When the device is connected to an IO-Link master through a 3-wire interface, the master can initiate communication and exchange data with the remote node, while the SN65HVD10X acts as a complete physical layer for the communication.

The IO-Link driver output (CQ) can be used in push-pull, high-side, or low-side configurations using the EN and TX input pins. The PHY receiver converts the 24-V IO-Link signal on the CQ pin to standard logic levels on the RX pin. The use of a simple parallel interface transmits and receives data and status information between the PHY and the local controller.

The SN65HVD101 and SN65HVD102 implement protection features for overcurrent, overvoltage, and overtemperature conditions. The IO-Link driver current limit can be set using an external resistor. If a short-circuit current fault occurs, the driver outputs are internally limited and the PHY generates an error signal (SC). These devices also implement an overtemperature shutdown feature that protects the device from high-temperature faults.



www.ti.com Block Diagram

The SN65HVD102 operates from a single external 3.3-V or 5-V local supply. The SN65HVD101 integrates a linear regulator that generates either 3.3 V or 5 V from the IO-Link L+ voltage for supplying power to the PHY, as well as a local controller and additional circuits.

The SN65HVD101 and SN65HVD102 are available in the 20-pin RGB package (4 mm × 3.5 mm quad flat no leads (QFN)) for space-constrained applications.

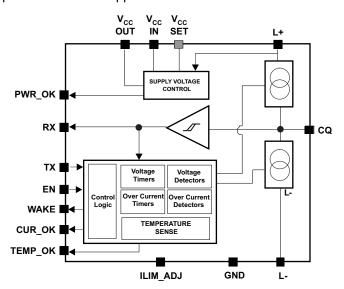


Figure 2. Functional Block Diagram SN65HVD102

- Configurable CQ output: push-pull, high-side, or low-side for SIO Mode
- · Remote wake-up indicator
- Current limit indicator
- Power-good indicator
- Overtemperature protection
- Reverse polarity protection
- Configurable current limits
- 9-V to 36-V supply range
- Tolerant to 50-V peak line voltage
- 3.3-V or 5-V configurable integrated LDO (SN65HVD101 only)
- 20-pin QFN package, 4 mm x 3.5 mm

3.1.2 TPS7A1633

The TPS7A16 family of ultra-low power, LDO voltage regulators offers the benefits of ultra-low quiescent current, high input voltage, and miniaturized, high thermal-performance packaging.

The TPS7A16 family is designed for continuous or sporadic (power backup) battery-powered applications where ultra-low quiescent current is critical to extending the system battery life.

The TPS7A16 family offers an enable pin (EN) compatible with standard complementary metal-oxide-semiconductor (CMOS) logic and an integrated, open-drain, and active-high power good output (PG) with a user-programmable delay. These pins are intended for use in microcontroller-based, battery-powered applications where power-rail sequencing is required.

In addition, the TPS7A16 is ideal for generating a low-voltage supply from multi-cell solutions ranging from high cell-count power-tool packs to automotive applications. Not only can this device supply a well-regulated voltage rail, but it can also withstand and maintain regulation during voltage transients. These features translate to simpler and more cost-effective, electrical surge-protection circuitry.



Block Diagram www.ti.com

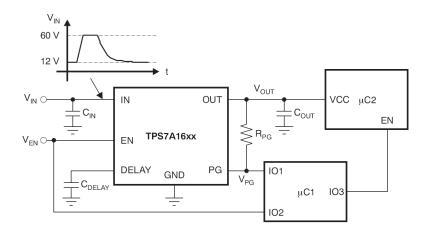


Figure 3. Functional Block Diagram TPS7A1633

Wide input voltage range: 3 V to 60 V
 Ultra-low quiescent current: 5 μA
 Quiescent current at shutdown: 1 μA

Output current: 100 mA

Low dropout voltage: 60 mV at 20 mA

Accuracy: 2%Available in:

Fixed output voltage: 3.3 V, 5.0 V

Adjustable version from approximately 1.2 V to 18.5 V

Power good with programable delay

- Current-limit and thermal shutdown protections
- Stable with ceramic output capacitors: ≥ 2.2 µF
- Package: high thermal performance MSOP-8 PowerPAD™
- Operating temperature range: –40°C to 125°C

3.1.3 MSP-EXP430FR4133

The MSP-EXP430FR4133 LaunchPad development kit is an easy-to-use evaluation module (EVM) for the MSP430FR4133 microcontroller. The development kit contains everything needed to start developing on the MSP430 ultra-low power (ULP) FRAM-based microcontroller platform, including on-board emulation for programming, debugging, and energy measurements. The board features on-board buttons and LEDs for the quick integration of a simple user interface as well as a liquid crystal display (LCD), which showcases the integrated driver with flexible software-configurable pins. The MSP430FR4133 device features embedded FRAM (ferroelectric random access memory), a non-volatile memory known for its ultra-low power, high endurance, and high-speed write access.

Rapid prototyping is simplified by the 20-pin BoosterPack plug-in module headers, which support a wide range of available BoosterPacks. Users can quickly add features like wireless connectivity, graphical displays, environmental sensing, and much more. Users can also design a customized BoosterPack or choose among many already available from TI and third-party developers.

The out-of-box functionality provided with the MSP-EXP430FR4133 LaunchPad features the on-board segmented display and offers two operating modes. Stop-Watch Mode can run a timer for up to 100 hours, or alternatively operate split time, where the display can be frozen and the stopwatch continues running in the background. The second mode, Operate Split Time, provides a simple thermometer application using the on-chip temperature sensor. The temperature is displayed on the LCD and can be shown in degrees Fahrenheit or Celsius.



www.ti.com Block Diagram

Free software development tools are also available, such as Tl's Eclipse-based Code Composer Studio™ software and IAR Embedded Workbench. Both of these integrated development environments (IDEs) support EnergyTrace™ technology when paired with the MSP430FR4133 LaunchPad. More information about the LaunchPad, the supported BoosterPacks, and available resources can be found at Tl's LaunchPad portal www.ti.com/launchpad.



Figure 4. MSP-EXP430FR4133 Board Picture

- MSP430 ULP FRAM-based MSP430FR4133 16-bit MCU 16KB FRAM
 - 16-Bit RISC architecture up to 8-MHz FRAM access and 16-MHz system clock speed
 - 3 x timer blocks
 - 10-ch 10-bit analog-to-digital converter (ADC)
 - 8 x 32 segment LCD driver with integrated charge pump and configurable pins
- EnergyTrace available for ultra-low power debugging
- 20-pin LaunchPad standard leveraging the BoosterPack ecosystem
- Onboard eZ-FET emulation
- Two buttons and two LEDs for user interaction.
- Segmented LCD

System Design Theory www.ti.com

4 System Design Theory

4.1 Power Supply

In an IO-Link based sensor transmitter, the sensor itself can draw power from the L+ line. While the SN65HVD101 has a built-in LDO with a 3.3-V or 5-V output to supply the remaining circuits, the SN65HVD102 requires its supply from an external source. Due to the modular approach and flexibility of this TI design, the on-board LDO TPS7A1633 device is used to supply the IO-Link PHY. For the overall sub-system evaluation (TIDA-00339 and MSP430 LaunchPad), the SN65HVD102 device can also be supplied by the 3.3 V from the LaunchPad.

Table 1 shows the three power supply options.

Table 1. TIDA-00339 Power Supply Options

TIDA-00339 POWER	R SUPPLY OPTIONS	J1	J2	COMMENTS
1	3.3 V from LaunchPad	X	-	The board gets its 3.3 V from the connected LaunchPad
2	3.3 V from TPS7A1633	-	X	The board gets its 3.3 V from the LDO (TPS7A1633)
3	3.3 V from TPS7A1633 while powering LaunchPad	Х	Х	The board gets its 3.3 V from the LDO (TPS7A1633) and the MCU of the connected LaunchPad is also powered by the LDO

CAUTION

Due to the use of a LaunchPad and its flexible design, the user must ensure that both boards (and additional booster packs) operate at the same voltage levels. Please carefully read the description of <u>power supply options</u> and the power section in the user's guide for the LaunchPad.

The MSP430 LaunchPad typically provides 3.3 V to the BoosterPack headers. To obtain the same voltage levels during TX and RX communication, and avoid voltage compliance issues at the MCUs GPIO pins, TI recommends to use either Power Supply Option 1 or Power Supply Option 3. While debugging the MCU (additional communication between the MCU and emulator), Power Supply Option 1 must be used. View the power supply options in Table 2:

Table 2. Power Supply Options

POWER SUPPLY OPTIONS	DESCRIPTION
	Remove jumper on J2; set jumper on J1.
1. 3.3 V from LP (DEFAULT)(1)	 Verify the power supply options of the connected LaunchPad and ensure that 3.3 V are provided at J12, Pin 1.
	Remove jumper on J1; set jumper on J2.
2. 3.3 V from TPS7A1633 ⁽²⁾	 Verify the power supply options of the connected LaunchPad to supply the MCU externally.
	Ensure that 3.3 V are provided at J12, Pin 1 from TPS7A1633.
3. 3.3 V from TPS7A1633 (which also powers the LaunchPad)(3)	Set jumper on J1; set jumper on J2.



www.ti.com System Design Theory

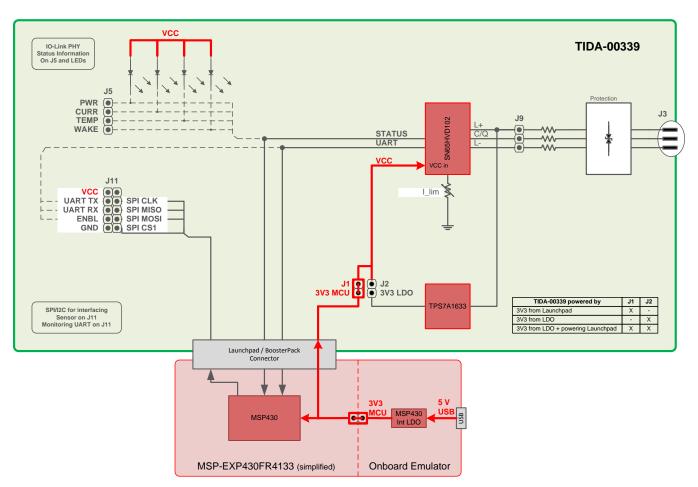


Figure 5. Power Supply—Option 1



System Design Theory www.ti.com

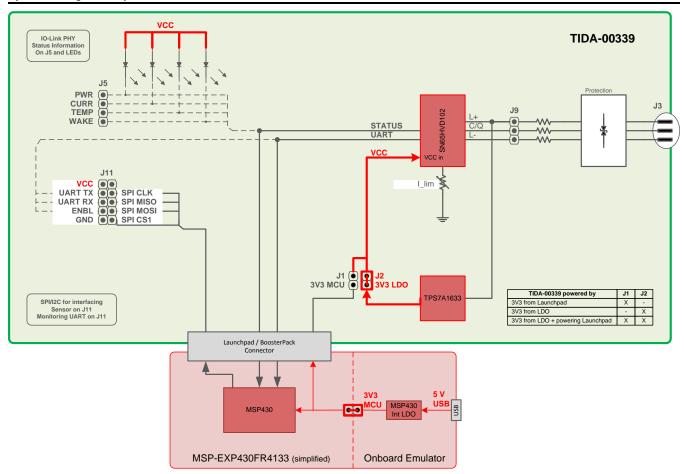


Figure 6. Power Supply—Option 2



www.ti.com System Design Theory

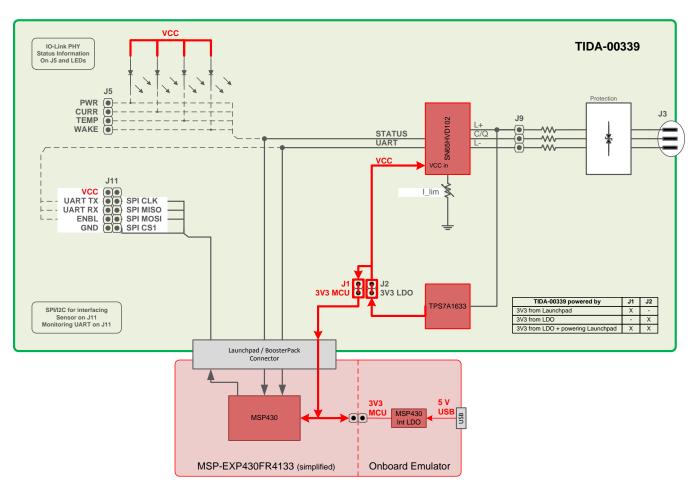


Figure 7. Power Supply—Option 3



System Design Theory www.ti.com

4.2 Protection

The L+ and CQ pins of the SN65HVD101 device offer a ±40-V absolute maximum steady voltage rating, which is furthermore extended to ±50 V for transients with a pulse width less than 100 μs.

The IO-Link PHY (U2) margin and the ability of the PHY to withstand even negative voltages ease the design because of the robustness of the solution against electrostatic discharge (ESD), burst, and surges as defined in the IEC 61000-4-2, IEC 6100-4-4, and IEC 6100-4-5 standards.

The design uses an additional transient protection circuitry consisting of the transient voltage suppressor (TVS) diodes (D4, D5, and D6) and bypass capacitors (C4, C5, and C7) to be in compliance with IEC 61000-4-2, IEC 6100-4-4, and IEC 6100-4-5 standards.

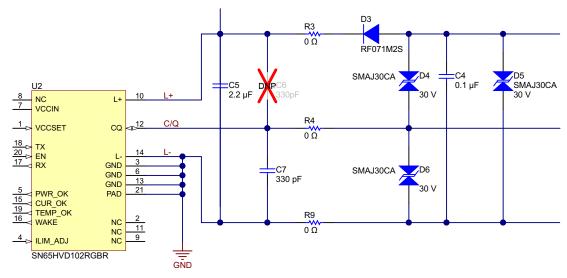


Figure 8. IO-Link Interface With Protection

The IO-Link specification does not require a surge transient test (IEC61000-4-5) because of the limitation of maximum cable length to 20 meters; however, use of the design in applications using digital input or output, and with cable lengths exceeding 30 meters, requires surge testing. The design uses the assumption that the surge test is the most severe of the three transient test cases. The design also uses the assumption that the surge test is the test with the highest energy level; therefore, take special care when selecting the right TVS as a clamping device.

www.ti.com System Design Theory

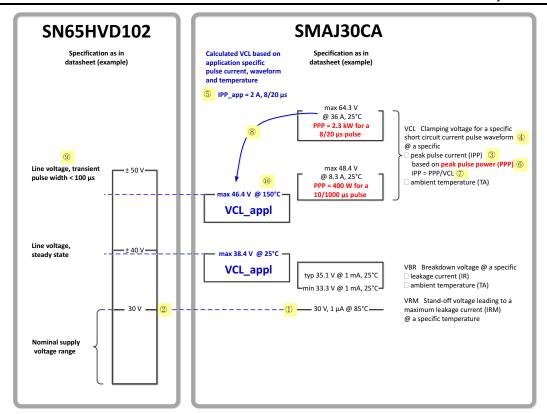


Figure 9. SN65HVD102 Device and SMAJ30CA Device

In order to choose TVS diodes appropriately, three requirements must be satisfied:

- 1. VRM is the stand-off voltage ① (the voltage when the TVS does not conduct). The VRM must be greater than or equal to the maximum signal of the transceiver and a supply voltage of 30 V ② to prevent the TVS from conducting during normal operation.
- 2. IPP, the peak pulse current of the TVS ③ at the short circuit pulse waveform, ④ must be greater than the application-specific peak pulse current IPP_app ⑤. The open circuit voltage of the combination wave generator (surge generator) and the impedance of the generator and the coupling device determines the application-specific peak pulse current IPP_app ⑤. Most TVSs specify the IPP for a 10/1000-µs pulse only; however, the pulse used for the surge test is mostly an 8/20-µs pulse. In this case, the pulse rating curve in the datasheet can be used to derive the peak pulse power PPP ⑥ for a specific pulse width of 20 µs. IPP can then be derived ⑦ by dividing the PPP by the estimated clamping voltage VCL at this IPP level. The VCL for an 8/20-µs pulse will be much larger than the VCL for the 10/1000-µs pulse. TI recommends to contact the TVS manufacturer when estimated values are used unless there is a large margin between IPP and IPP app.
- 3. When the TVS conducts and becomes low-impedance to shunt the surge current to ground, the TVS application-specific clamping voltage VCL_appl ® must be lower than the maximum transient stand-off voltage ® of ±50 V of the transceiver. To obtain the application specific clamping voltage, the VCL of the TVS must be reduced according to the reduction of the IPP to the application specific IPP_app. Some data sheets provide the differential resistance for the specific pulse waveform, which helps to determine the reduction of the IPP to the application specific IPP_app. If differential resistance for the specific pulse waveform is not supplied (and if there is not enough margin), contact the TVS manufacturer. The VBR and VCL voltages in the TVS data sheets are often given for an ambient temperature of 25°C only. Because those voltages usually have a positive temperature coefficient, the VCL values must be corrected accordingly to ensure that this requirement 3 is fulfilled, even at the maximum ambient temperature of the application specific case and under the conditions of multiple repetitive surges, which heat up ® the TVS. The temperature coefficient is given in most data sheets.



System Design Theory www.ti.com

For this IO-Link design, a 1.2 μs / 50 μs 1-kV pulse applied by way of a 500- Ω impedance has been considered according to IEC 60255-5. The resulting peak current through the clamping device (TVS) is then roughly 1 kV / 500 Ω = 2 A . The SMAJ30CA device is a bidirectional TVS and fulfills the above mentioned requirements by clamping voltages with both polarities. The SMAJ30CA device has a stand-off voltage (VRM) of 30 V, a minimum breakdown voltage (VBR) of 33.3 V, and an application specific clamping voltage of roughly 46.3 V at the 2-A current level and at a junction temperature of 150°C.

D3 provides an additional level of reverse polarity protection. While the SN65HVD102 device can withstand negative voltages up to -40 V (in steady state) and up to -50 V (transient) as expressed previously, the diode avoids the supply voltage bypass capacitor C5 being discharged during a negative pulse. The diode enables the design to recover much faster from such a negative surge event.

For testing purposes, the design allows to bypass the protection circuit. In this case the 0R resistors R3, R4, and R9 must be removed. The signals L+, L-, and C/Q cannot be fed through the M12 connector J3, but through the header J9. In this condition, the TVS diodes (D4, D5, and D6) and the reverse polarity diode D3 are no longer active.

4.3 Manual SIO Mode

The SIO Mode can either be used through the MCU (default) or manual operation. For manual operation, the shunts must be placed on J6 and J7 between PINs 2-3. With J8 the user can select between the NPN (1-2) or PNP (2-3) output. Switch button S2 can then be used for manual SIO Mode operation. Figure 10 is showing the circuit section. By using the manual SIO Mode, the signals TX and EN of the IO-Link PHY (U2) are disconnected from the MCU on the LaunchPad.

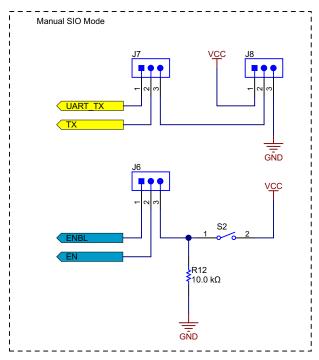


Figure 10. Manual SIO Mode



www.ti.com System Design Theory

4.4 Interfacing MCU

TIDA-00339 is designed as a BoosterPack in order to be used with TI's LaunchPads. Because the IO-Link communication requires an IO-Link PHY (U2) in addition to the MCU for the stack, the user can choose from different MCUs for their needs. For this design guide, the LaunchPad MSP-EXP430FR4133 has been chosen for verification.

Figure 11 shows the standardized pinout of the different available LaunchPads. Figure 12 shows the two connectors J10 and J12 to connect the IO-Link design to the LaunchPad. An overview of the connection between TIDA-00339 and the LaunchPad is given in Figure 11.

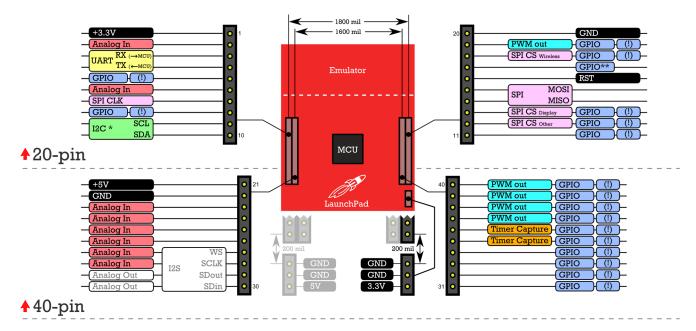


Figure 11. BoosterPack Pinout

Table 3. Pin Description of MSP-EXP430FR4133 LaunchPad and TIDA-00339

LAUNCHPAD		TIDA-	TIDA-00339	
PINs	DESCRIPTION	PINs J12	DESCRIPTION	FUNCTION
1	3.3V	1	3V3	VCC from LP (BP) to BP (LP) – Depending on the power settings
2	Analog In	3	-	
3	UART RX	5	UART RX	Communication between MCU on LaunchPad and SN65HVD102
4	UART TX	7	UART TX	Communication between MCU on LaunchPad and SN65HVD102
5	GPIO	9	ENBL	Communication between MCU on LaunchPad and SN65HVD102
6	Analog In	11	-	
7	SPI CLK	13	SPI_CLK	SPI clock for the communication between MCU on LP and an optionally connected sensor
8	GPIO	15	CUR_OK	STATUS signal from SN65HVD102
9	I2C SCL	17	-	



System Design Theory www.ti.com

Table 3. Pin Description of MSP-EXP430FR4133 LaunchPad and TIDA-00339 (continued)

PINs (CONTINUED)	DESCRIPTION	PINs J10	DESCRIPTION	FUNCTION
10	I2C SDA	19	-	
22	GND	4	GND	
20	GND	2	GND	
19	GPIO	4	TEMP_OK	STATUS signal from SN65HVD102
18	SPI CS	6	SPI_CS1	
17	GPIO	8	SW	General purpose switch S1 (that is, the teaching function)
16	RST	10	-	
15	SPI MOSI	12	SPI_MOSI	SPI for the communication between MCU on LP and an optionally connected sensor
14	SPI MISO	14	SPI_MISO	SPI for the communication between MCU on LP and an optionally connected sensor
13	GPIO	16	LED	General purpose LED (that is, status indication)
12	GPIO	18	PWR_OK	STATUS signal from SN65HVD102
11	GPIO	20	WAKE	STATUS signal from SN65HVD102

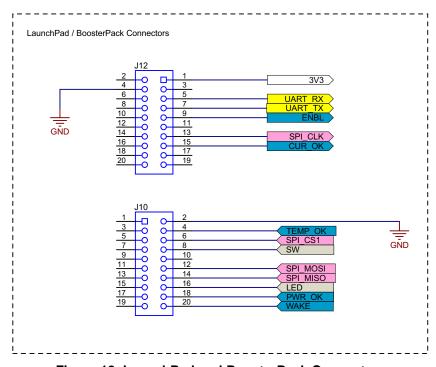


Figure 12. LaunchPad and BoosterPack Connectors

www.ti.com System Design Theory

4.5 Interfacing Sensor Front-End

In addition to evaluating the IO-Link interface with different MCUs, the design also enables the user to attach a sensor front-end, allowing testing of an overall system. A sensor front-end can be connected in two ways, through an SPI and by choosing the I²C interface (depending on the type of LaunchPad used):

- J10 and J12 The SPI signals from the MCU on the LaunchPad are available on J10 and J12 (LaunchPad and BoosterPack connectors) and another BoosterPack can be connected with a sensor front-end.
- 2. J11 The SPI signals from the MCU on the LaunchPad, which are present on J10 and J12, are also routed to J11 for easy access, as Figure 13 shows.

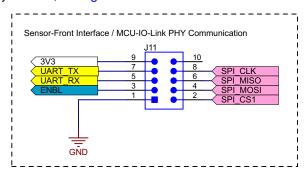


Figure 13. Sensor-Front Interface and MCU-IO-Link PHY Communication

4.6 C/Q Current Limiter

The C/Q driver output current limit of SN65HVD102 can be set using an external resistor on the LIMADJ pin. This limit can typically be set between 95 mA for a resistor of 20 k and 400 mA for a 0R resistor. Figure 14 shows the non-linear behavior between resistor value and current limit.

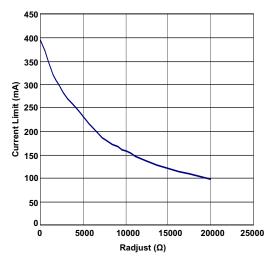


Figure 14. Typical Current Limit Characteristics

The design has the flexibility to adjust the current limit with the potentiometer R11 (Figure 15) or use the default resistor value of R10 = 4.75 k (approximately 250 mA, typically).

Table 4. Settings for the Current Limiter Options

J4	RESISTOR	DESCRIPTION
PINs 1-2 shorted	R11 active	20-k potentiometer M flexible adjustment of C/Q current limit
PINs 2-3 shorted (default)	R10 active	4.75-k resistor M 250 mA



System Design Theory www.ti.com

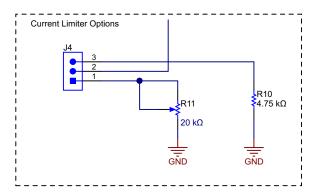


Figure 15. Current Limiter Options



www.ti.com Getting Started

5 Getting Started

5.1 Board Description

Figure 16 shows the different sections of the TIDA-00339 design.

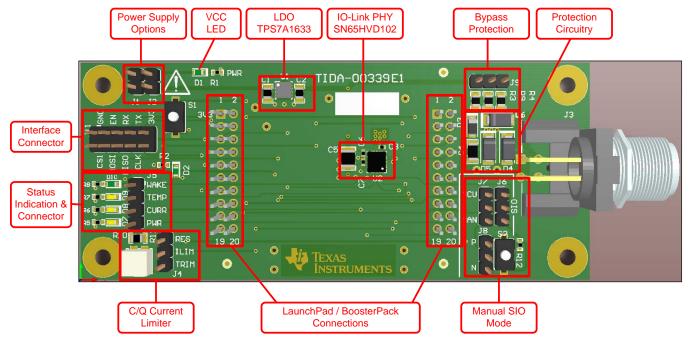


Figure 16. TIDA-00339 Board Description

Power supply options

As described in Section 4.1, the design has several power supply options depending on the usage. Table 5 shows the different settings of J1 and J2. For the initial setup, use Power Supply Option 2.

TIDA-00339 POWER	TIDA-00339 POWER SUPPLY OPTIONS		J2	COMMENTS
1	3.3 V from LaunchPad	Х	-	The board gets its 3.3 V from the connected LaunchPad
2	3.3 V from TPS7A1633	-	Х	The board gets its 3.3 V from the LDO (TPS7A1633)
3	3.3 V from TPS7A1633 while powering LaunchPad	Х	х	The board gets its 3.3 V from the LDO (TPS7A1633) and the MCU of the connected LaunchPad is also powered by the LDO

Table 5. Power Supply Options

VCC LED

LED D1 indicates the presence of VCC.

LDO - TPS7A1633

The linear voltage regulator circuit (in Power Supply Option 2 and Power Supply Option 3) generates the 3.3-V VCC from the 24 V of the IO-Link interface.



Getting Started www.ti.com

IO-Link PHY - SN65HVD102

Circuitry of the IO-Link PHY.

Bypass protection

The user can bypass the on-board protection circuit by removing R3, R4, and R9. The entire protection is removed, including M12 connector J3, and the IO-Link signals L+, L-, and C/Q must be applied through J9. Note that in this case the reverse polarity is no longer available.

Protection circuitry

The design uses an additional transient protection circuitry consisting of the TVS diodes (D4, D5, and D6) and bypass capacitors (C4, C5, and C7) to be in compliance with the IEC 61000-4-2, IEC 6100-4-4, and IEC 6100-4-5 standards. Refer to Section 4.2 for more details on the protection circuitry.

Manual SIO Mode

Section to enable the manual SIO Mode and use switch S2 to toggle either NPN or PNP.

Table 6. SIO Mode Options

J6	J7	J8	DESCRIPTION
1-2	1-2	X	MCU control
2-3	2-3	1-2	Manual S2 control, NPN Mode
2-3	2-3	2-3	Manual S2 control, PNP Mode

LaunchPad and BoosterPack connectors

J10 and J12 are the connectors to interface TIDA-00339 to a LaunchPad. Please refer to the LaunchPad in use to ensure proper connection between the devices. J10 and J12 have two long pins allowing the connection of additional BoosterPacks on top of the TIDA-00339 device; for example, a display BoosterPack or a sensor front-end BoosterPack.

C/Q current limiter

The circuitry changes between the resistor R10 (4.75 k) and potentiometer R11 (20 k) to allow individual settings of the current limit of the C/Q line.

Table 7. Settings for Current Limit Options

J4	RESISTOR	DESCRIPTION
PINs 1-2 shorted	R11 active	20-k potentiometer → flexible adjustment of C/Q current limit
PINs 2-3 shorted (default)	R10 active	4.75-k resistor → 250 mA

Status indication and connector

The status signals of the IO-Link PHY WAKE, TEMP OK, CURR OK, and PWR OK are available on J5 and indicated with LEDs D7, D8, D9, and D10. The output of those signals is an open drain output. In case of a fault operation (warning or error) the GND switches to the respective J5 pins and the corresponding LEDs illuminate. During normal operation the LEDs must be off.

Interface connector

The interface connector J11 can be used to connect an additional sensor front-end to the SPI of the MCU of the connected LaunchPad. Connector J11 also monitors the communication interface between the IO-Link PHY and the MCU. See Section 4.6 for more details.



www.ti.com Getting Started

5.2 First Board Setup Manual SIO Mode

The initial board setup uses the TIDA-00339 in manual SIO Mode without the need of a connected LaunchPad. In this mode, IO-Link communication is impossible.

Table 8. Jumper Setting for First Board Setup

JUMPER	SHORT	COMMENTS
J1	Remove	Dower Supply Option 2 enabled
J2	Set 1-2	Power Supply Option 2 enabled
J4	Set 2-3	Resistor R10 (4.75k) active
J6	Set 2-3	Manual SIO Mode active
J7	Set 2-3	Maridal SIO Mode active
J8	Set 1-2	NPN selected

5.3 First Board Setup IO-Link Mode

5.3.1 Hardware and Software Requirements

For the initial setup the following hardware and software is required:

- TIDA-00339
- MSP-EXP430FR4133 LaunchPad
 - IO-Link stack including the application firmware (4)
- USB IO-Link Master (this design uses the TMG USB IO-Link Master V2 SE)
 - GUI for USB IO-Link Master (this design uses the TMG IO-LINK Device Tool V4.0)
- IO Device Description (IODD) (4)
- M12 cable (female male)
- USB cable

5.3.2 Software Installation

Please refer to the user manual of the USB IO-Link master in use for further details on its software installation and how to import the IODD folder.

The following steps use the USB IO-Link Master V2 SE software from TMG (www.tmgte.com). The user manual is available after installing the software, which is delivered along with the hardware. The user manual describes the steps involved in importing the IODD files.



Getting Started www.ti.com

5.3.3 Step-By-Step Description

1. Verify the jumper settings of the TIDA-00339 device (Table 9). Use the Power Supply Option 1 (3.3 V for TIDA-00339 is provided by the LaunchPad).

Table 9. Jumper Settings for Board Setup in IO-Link Mode

JUMPER	SHORT	COMMENTS	
J1	Set 1-2	Power Supply Option 1 enabled	
J2	Remove	Power Supply Option 1 enabled	
J4	Set 2-3	Resistor R10 (4.75 k) active	
J6	Set 1-2	IO Link Made active	
J7	Set 1-2	IO-Link Mode active	
J8	Don't Care	Only active in Manual SIO Mode	

2. Verify the jumper settings of the LaunchPad (Table 10). This example uses the MSP-EXP430FR4133 LaunchPad. Please refer to the user's guide of the LaunchPad in use for more details.

Table 10. Jumper Settings for MSP-EXP430FR4133 LaunchPad

CONNECTOR	JUMPER (SILKSCREEN)	SHORT
JP1	JP1	Set 1-2
J101	GND	Set
J101	5V	Set
J101	3V3	Set
J101	RTS	Remove
J101	CTS	Remove
J101	RXD	Set
J101	TXD	Set
J101	SBWTDIO	Set
J101	SBWTCK	Set

3. As Figure 17 shows, connect the TIDA-00339 device (J10 and J12 outer rows) to the MSP-EXP430FR4133 device (J1 and J2).

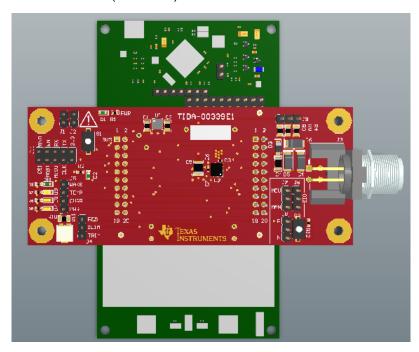


Figure 17. Connection Between TIDA-00339 and MSP-EXP430FR4133



www.ti.com Getting Started

4. Connect the PC through a USB cable to the LaunchPad J102 to power the system. If the LaunchPad is not pre-programmed, please refer to the Software Section of the TIDA-00339 product folder (4).

- 5. Verify that the LED D1 of TIDA-00339 is on as soon as the system powers on.
- 6. Connect the TIDA-00339 (J3) to the IO-Link master.
- 7. Launch the USB IO-Link Master V2 software on the PC.
- 8. Follow the steps provided in the IO-Link Master user's manual to establish a connection and import the IODD files.
- 9. Figure 18 shows a screen-shot of the GUI after successfully establishing the connection.
- 10. Figure 19 shows the Process Data tab, which shows the content of the available variables.

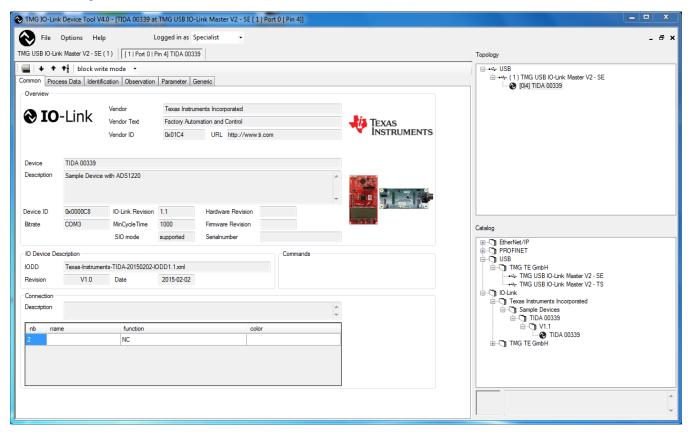


Figure 18. IO-Link Master GUI After Established Connection to TIDA-00339



Getting Started www.ti.com

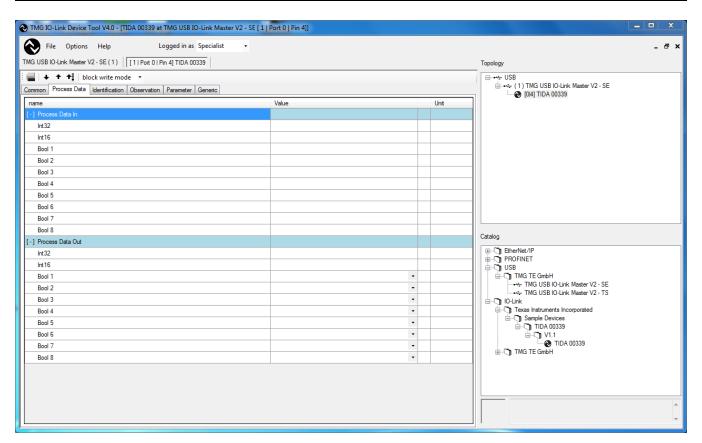


Figure 19. IO-Link Master GUI—Process Data Tab

5.3.4 Usage

To reiterate, the objective of this TI design is to allow a flexible evaluation of the IO-Link interface with the existing sensor front-ends. A connectable sensor front-end requires an MCU because of the flexibility of the TIDA-00339 device. This MCU communicates with the MSP430 on the LaunchPad, exchanging the data from the sensor to the IO-Link interface and vice versa (for configuring the sensor). Several variables are available for this communication (INT32, INT16, and Bool1 to Bool8).

The default application "Stop-Watch" has been modified in the MSP-EXP430FR4133 firmware.

- 1. Stop-Watch Mode: The LaunchPad runs its default application "Stop-Watch" and the data sends through the IO-Link interface to the IO-Link master and displays in the GUI. The sensor front-end is not used in Stop-Watch Mode.
- Temperature Mode: The LaunchPad runs its default application "Temperature" and the data sends through the IO-Link interface to the IO-Link master and displays in the GUI. The sensor front-end is not used in Temperature Mode.
- 3. Sensor Front-End Mode: The LaunchPad runs the additional "Sensor" and sends the data through the IO-Link interface to the IO-Link master and displays the data in the GUI. A sensor front-end is required in the Sensor Front-End Mode.



Design Files www.ti.com

Design Files 6

6.1 Schematic

To download the schematic, see the design files at TIDA-00339.

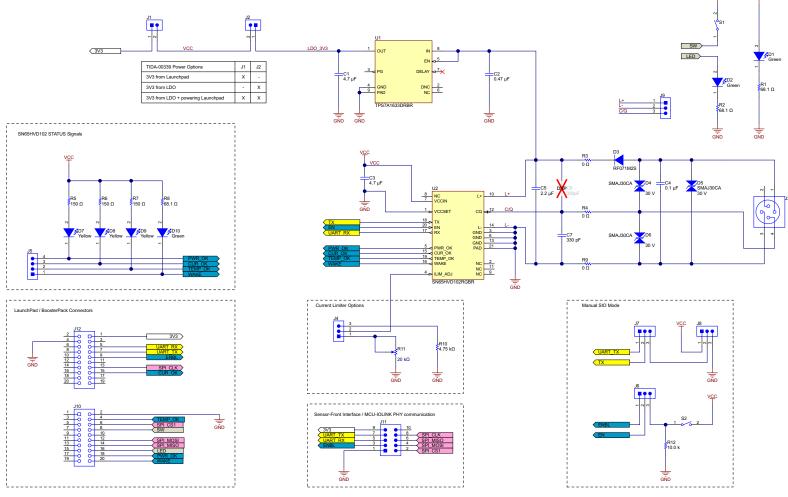


Figure 20. Schematic



Design Files www.ti.com

6.2 Bill of Materials

To download the bill of materials (BOM), see the design files at TIDA-00339.

Table 11. BOM

ITEM #	DESIGNATOR	QUANTITY	VALUE	PART NUMBER	MANUFACTURER	DESCRIPTION	PACKAGE REFERENCE
1	!PCB1	1		TIDA-00339	Any	Printed Circuit Board	
2	C1	1	4.7 μF	GRM21BR71A475KA73L	MuRata	CAP, CERM, 4.7 μF, 10 V, ±10%, X7R, 0805	0805
3	C2	1	0.47 µF	GRM21BR72A474KA73L	MuRata	CAP, CERM, 0.47 μF, 100 V, ±10%, X7R, 0805	0805
4	C3	1	4.7 μF	C1005X5R0J475M050BC	TDK	CAP, CERM, 4.7 μF, 6.3 V, ±20%, X5R, 0402	0402
5	C4	1	0.1 μF	12061C104JAT2A	AVX	CAP, CERM, 0.1 μF, 100 V, ±5%, X7R, 1206	1206
6	C5	1	2.2 µF	GRM32ER72A225KA35L	MuRata	CAP, CERM, 2.2 μF, 100 V, ±10%, X7R, 1210	1210
7	C7	1	330 pF	GRM155R72A331KA01D	MuRata	CAP, CERM, 330 pF, 100 V, ±10%, X7R, 0402	0402
8	D1, D2, D10	3	Green	150060VS75000	Wurth Elektronik eiSos	LED, Green, SMD	LED_0603
9	D3	1	200 V	RF071M2S	Rohm	Diode, Ultrafast, 200 V, 1 A, SOD- 123	SOD-123
10	D4, D5, D6	3	30 V	SMAJ30CA	Littelfuse	Diode, TVS, Bi, 30 V, 400 W, SMA	SMA
11	D7, D8, D9	3	Yellow	150060YS75000	Wurth Elektronik eiSos	LED, Yellow, SMD	LED_0603
12	FID1, FID2, FID3	3		N/A	N/A	Fiducial mark. There is nothing to buy or mount.	Fiducial
13	J1, J2	2		61300211121	Wurth Elektronik eiSos	Header, 2.54 mm, 2 x 1, Gold, TH	Header, 2.54 mm, 2 x 1, TH
14	J3	1		43-01205	Conec	M12 Socket, Backmounting, 4Pos, Gold, R/A, TH	M12 Socket, Backmounting, 4Pos, R/A, TH
15	J4, J6, J7, J8, J9	5		61300311121	Wurth Elektronik eiSos	Header, 2.54 mm, 3 x 1, Gold, TH	Header, 2.54 mm, 3 x 1, TH
16	J5	1		61300411121	Wurth Elektronik eiSos	Header, 2.54 mm, 4 x 1, Gold, TH	Header, 2.54 mm, 4 x 1, TH
17	J10, J12	2		SSW-110-23-F-D	Samtec	Connector, Receptacle, 100 mil, 10 x 2, Gold plated, TH	10 x 2 Receptacle
18	J11	1		61301021121	Wurth Elektronik eiSos	Header, 2.54 mm, 5 x 2, Gold, TH	Header, 2.54 mm, 5 x 2, TH
19	R1, R2, R8	3	68.1	CRCW040268R1FKED	Vishay-Dale	RES, 68.1, 1%, 0.063 W, 0402	0402
20	R3, R4, R9	3	0	CRCW08050000Z0EAHP	Vishay-Dale	RES, 0, 5%, 0.333 W, 0805	0805
21	R5, R6, R7	3	150	CRCW0402150RFKED	Vishay-Dale	RES, 150, 1%, 0.063 W, 0402	0402



Design Files www.ti.com

Table 11. BOM (continued)

ITEM #	DESIGNATOR	QUANTITY	VALUE	PART NUMBER	MANUFACTURER	DESCRIPTION	PACKAGE REFERENCE
22	R10	1	4.75 kΩ	CRCW08054K75FKEA	Vishay-Dale	RES, 4.75 kΩ, 1%, 0.125 W, 0805	0805
23	R11	1	20 kΩ	3224J-1-203 E	Bourns	TRIMMER, 20 kΩ, 0.25 W, SMD	4.8 x 3.71 x 4.6 mm
24	R12	1	10.0 kΩ	CRCW040210K0FKED	Vishay-Dale	RES, 10.0 kΩ, 1%, 0.063 W, 0402	0402
25	S1, S2	2		434121025816	Wurth Elektronik eiSos	Switch, Tactile, SPST, 12 V, SMD	SMD, 6 x 3.9 mm
26	U1	1		TPS7A1633DRBR	Texas Instruments	60-V, 5-μA IQ, 100-mA, Low-Dropout Voltage Regulator With Enable and Power-Good, DRB0008B	DRB0008B
27	U2	1		SN65HVD102RGBR	Texas Instruments	IO-LINK PHY for Device Nodes, RGB0020A	RGB0020A
28	C6	0	330 pF	GRM155R72A331KA01D	MuRata	CAP, CERM, 330 pF, 100 V, ±10%, X7R, 0402	0402



Design Files www.ti.com

6.3 Layer Plots

To download the layer plots, see the design files at TIDA-00339.

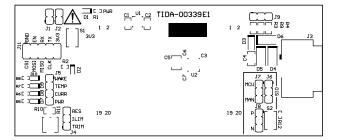


Figure 21. Top Overlay

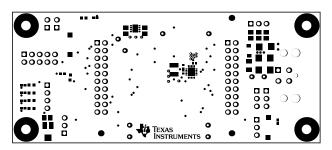


Figure 22. Top Solder Mask

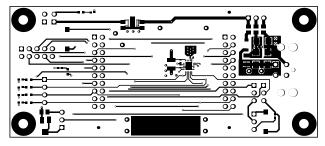


Figure 23. Top Layer

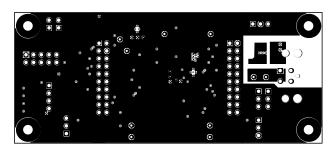


Figure 24. Midlayer 1

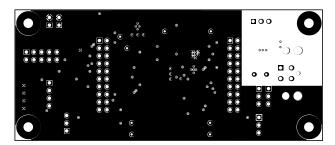


Figure 25. Midlayer 2

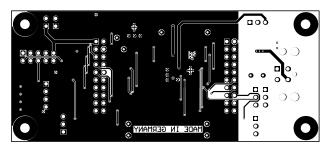


Figure 26. Bottom Layer

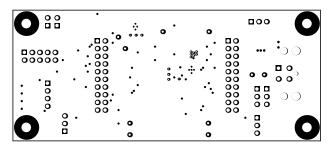


Figure 27. Bottom Solder Mask

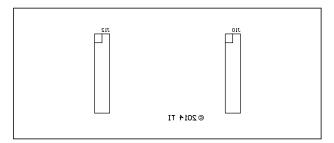


Figure 28. Bottom Overlay



www.ti.com Design Files

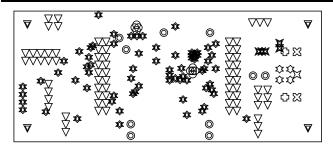




Figure 29. Drill Drawing

Figure 30. Board Outline



Design Files www.ti.com

6.4 Assembly Drawings

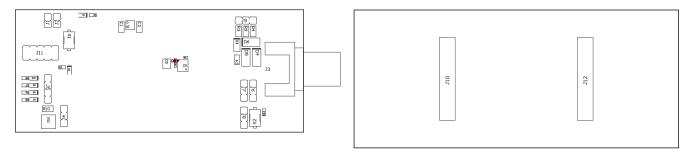


Figure 31. Top Assembly Drawing

Figure 32. Bottom Assembly Drawing

6.5 PCB and Layout Guidelines

The form-factor of the PCB has been chosen to fit on existing MSP430 LaunchPads. The PCB of the TIDA-00339 device extends to the left and right sides instead of the top and bottom sides. This setup allows the user to operate any existing buttons and visual indicators like LEDs and displays on the LaunchPad. Figure 33 shows a 3D plot of the TI design connected to the MSP430 LaunchPad.

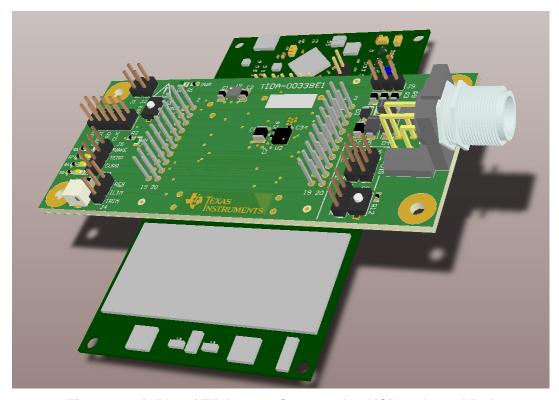


Figure 33. 3D-Plot of TIDA-00339 Connected to MSP430 LaunchPad



www.ti.com Software Files

TI recommends to place the protection circuitry close to the M12 connector (J3). The TVS diodes D4, D5, and D6 have been placed directly at J3, which enables the immediate clamping of potential high currents, according to the TVS specifications. Figure 34 shows a circuit snippet highlighting the three signals L+, L-, and C/Q going from J3 to the TVS diodes. In this view, the VCC and GND plane, as well as the polygons, were disabled.

Depending on the use for SN65HVD101 (U2), a proper thermal design is required, especially when the device is used in the SIO Mode. According to the datasheet, a residual voltage across the driver low-side switch of 3.5 V can be present for a current of 250 mA, resulting in a power dissipation of 875 mW.

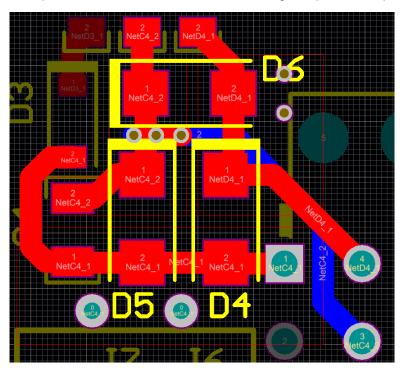


Figure 34. Layout of the Protection Circuitry

7 Software Files

To download the software files, see the design files at TIDA-00339.

8 About the Author

ALEXANDER WEILER is a systems engineer at Texas Instruments, where he is responsible for developing reference design solutions for the industrial segment. Alexander brings to this role his extensive experience in high-speed digital, low-noise analog, and RF system-level design expertise. Alexander earned his diploma in electrical engineering (Dipl.-Ing. (FH)) from the University of Applied Science in Karlsruhe, Germany.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.